


# Assembling the RPi-DAC (rev. 4)

For the parts - please see the list (BOM)


**Torsten Jaekel**  
[tj@tjaekel.com](mailto:tj@tjaekel.com)

November 2013

# PCB Fix - before soldering parts

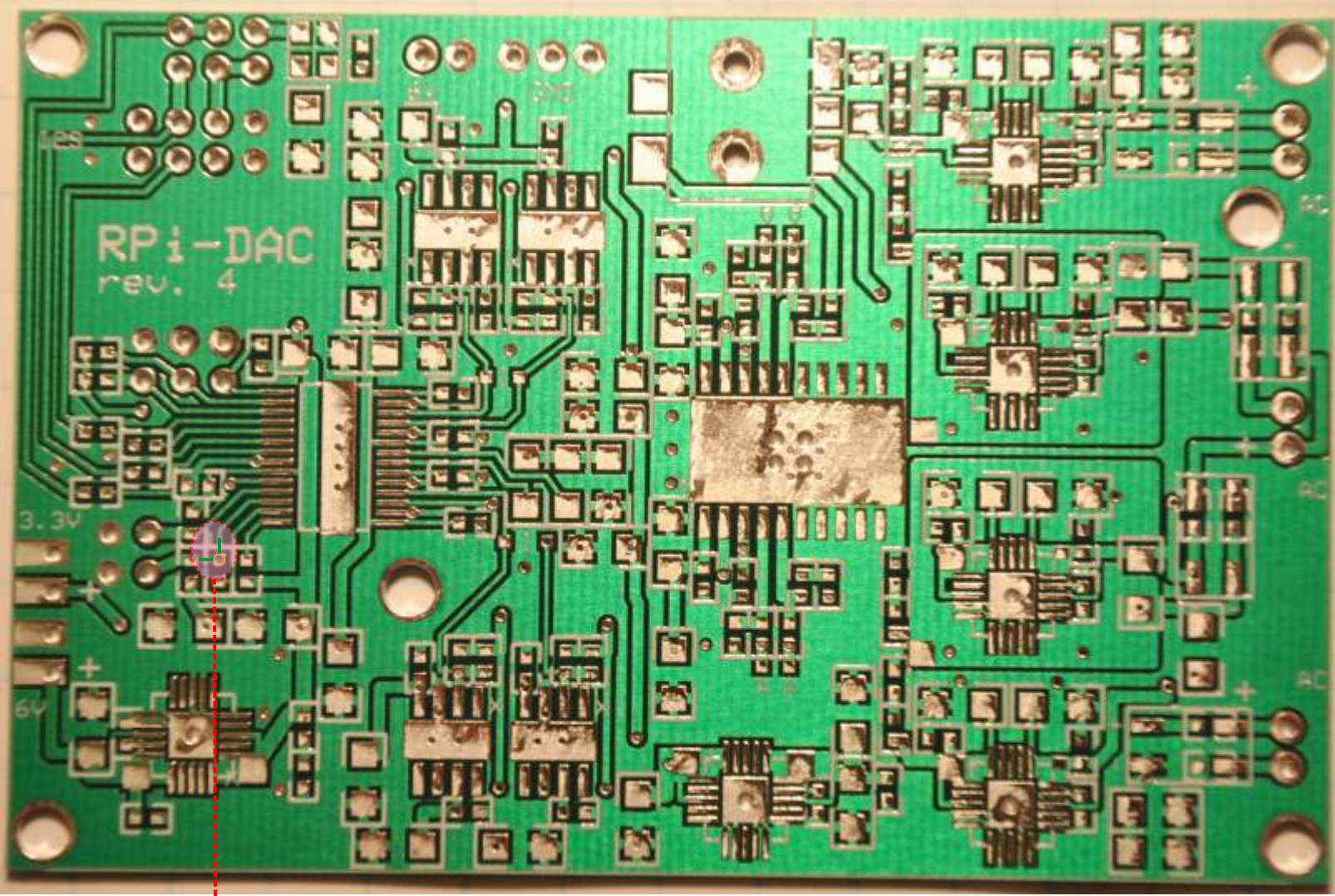

wire fix

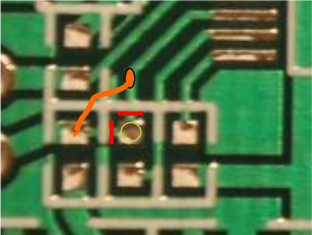


cut traces

# RPi-DAC

(rev. 4)


**option 1:**  
AC input,  
not using SPS

**Top**

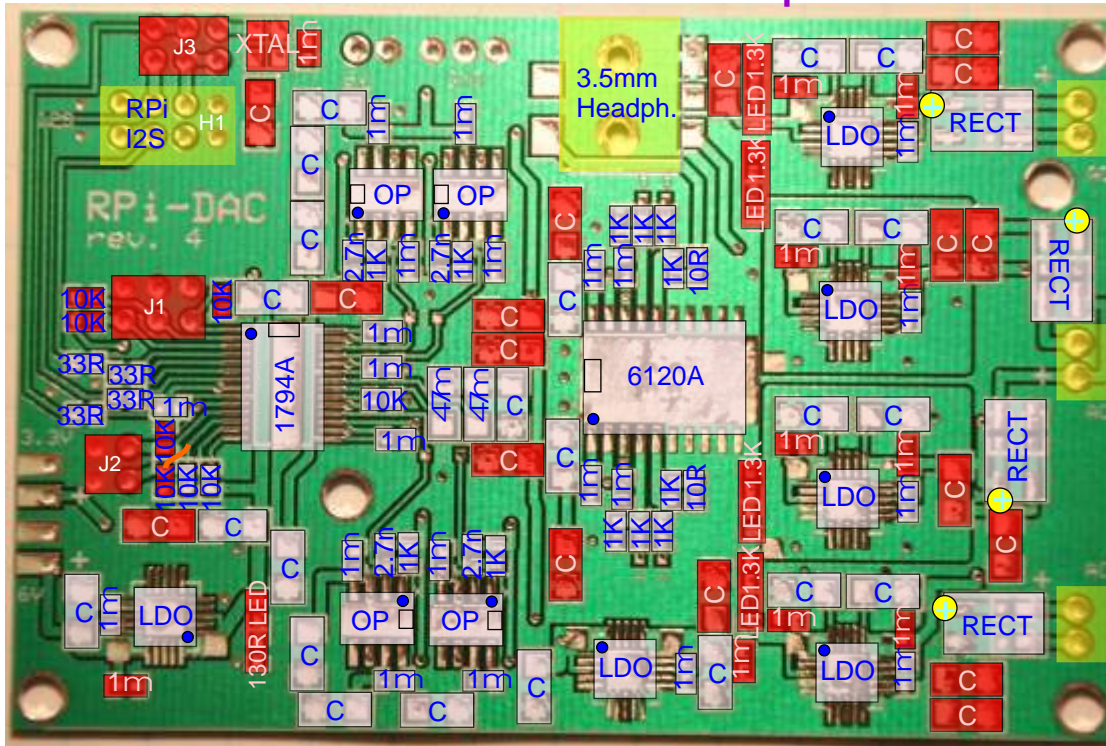

**option 3:**  
not J1, J2  
use 0R

**Bottom**

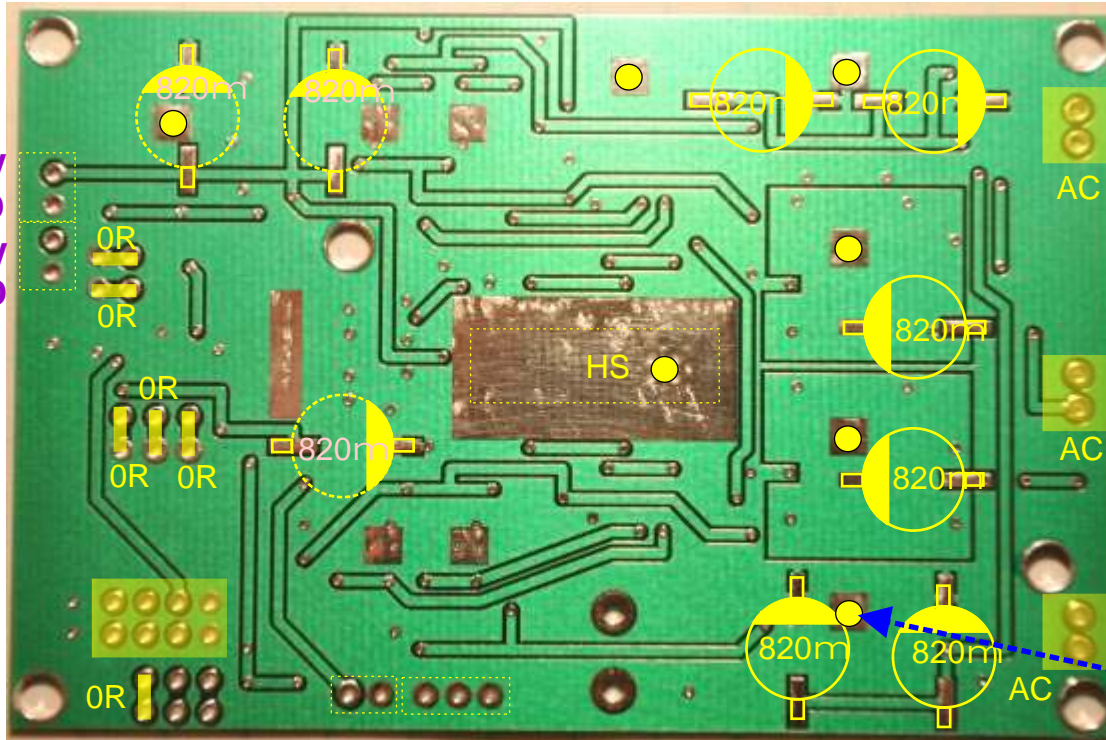

out: Headphone

out: 6V  
GND  
out: 3.3V  
GND

out: 6V GND

<span style="color: red;">■</span>	optional, not soldered
<span style="border: 1px dashed black; display: inline-block; width: 10px; height: 10px;"></span>	mandatory 22- 47m(24x)
C	(optional) 22- 47m(17x)
OP	LME49990 (4x)
LDO	TPS7A4700 (6x)
RECT	60V/2A Bridge (4x)
1794A	PCM1794A (1x)
6120A	TPA6120A (1x)
47m	(2x)
1m	mandatory (23x)
1m	(optional: RF blocking, 11x)
27n	(with 4x 1K)
1K	(8x)
10K	(3x, 5x optional with 0R jumper)
1K	(4x, with 2.7n)
33R	(4x)
10R	(2x)
0R	(6x, or Header with Jumpers, J1...J3)
820m	(6x, backside, 3x optional)
LED	(optional) yellow/green (2.0V) (5x plus R (10 mA))
H	(3x 2x1. 3x opt., 1x 3x1 optional)
H1	(female, 2x4 or I2S RPi)

**IN: >6V AC / 8V DC**

mount AC connectors on bottom side of PCB, if stacked with RPi or if using SPS

**IN: >12V AC / 17V DC**

use transformer with separate coils, no center tap for the +/- 15V

**IN: >12V AC / 17V DC**

solder PowerPad after LDOs mounted and checked


# RPi-DAC

(rev. 4)

**option 2:**  
DC input,  
with SPS

**Top**

**option 3:**  
not J1, J2  
use 0R

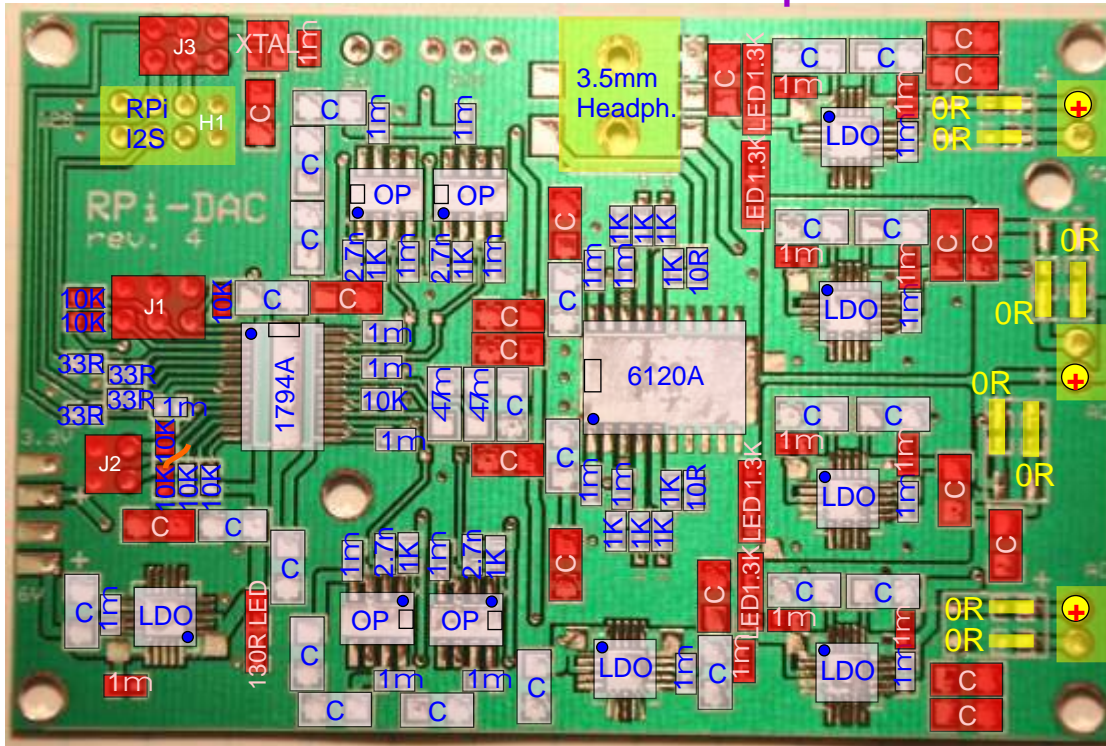

out: Headphone

<span style="color: red;">■</span>	<span style="border: 1px dashed black; display: inline-block; width: 10px; height: 10px;"></span>	optional, not soldered
C		mandatory 22- 47m(24x)
C		(optional) 22- 47m(17x)
OP		LME49990 (4x)
LDO		TPS7A4700 (6x)
0R		(8x, no RECT)
1794A		PCM1794A (1x)
6120A		TPA6120A (1x)
47m		(2x)
1m		mandatory (23x)
1m		(optional: RF blocking, 11x)
27n		(with 4x 1K)
1K		(8x)
10K		(3x, 5x optional with 0R jumper)
1K		(4x, with 2.7n)
33R		(4x)
10R		(2x)
0R		(6x, or Header with Jumpers, J1..J3)
LED		(optional) yellow/green (2.0V) (5x) plus R (10 mA)
H		(3x 2x1. 3x opt., 1x 3x1 optional)
H1		(female, 2x4 or I2S RPi)

**IN: 7V DC**

mount AC connectors on bottom side of PCB, if stacked with RPi or if using SPS


**IN: 16V DC**

do not have common GND for the + / - 15V

**IN: 16V DC**

solder PowerPad after LDOs mounted and checked

**Bottom**

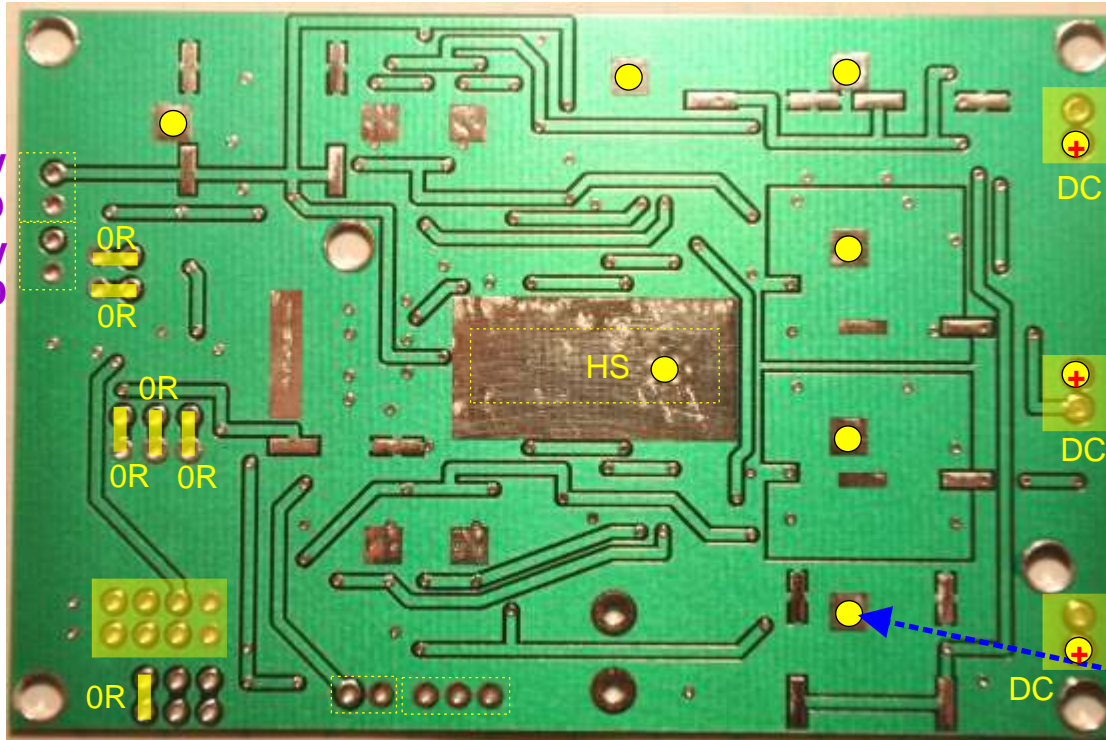


out: 6V  
GND  
out: 3.3V  
GND

out: 6V GND

# Order to solder the parts

1. Solder the **LDOs with the related Caps and Rectifier first** (details about LDO soldering see next page)
2. After soldering LDOs - check the LDOs. Do it for every LDO independently after one soldered:
  - apply AC or DC on AC connector (use a laboratory supply with current limiter)
  - measure output voltage (pin 1 and 20)
  - check if LDO regulates (keeps voltage quite constant on >15.6 V in, vary voltage on AC input)
  - check if regulation is stable, not oscillating or changing voltage randomly (esp. not following  $V_{in}$ )
3. If all LDOs are working properly, all board internal voltages 3.3V, 5V, +15V (2x) and -15V (2x) are correct then solder all remaining passive parts ( C and R, headers, jumpers connectors except H1 )
4. Check voltages again (maybe also current, should be in range of the LEDs, in range of >10 mA).
5. Solder the active ICs as the last parts. Before doing it, you could cross check if the supply voltages are correct on the related IC pins.
  - Solder the H1 female header (2x4) after all is ready to be stacked with RPi (see below).
6. If you provide now AC - **never let one +15 or -15V rail unpowered !** It will kill the OPs or AMP.
  - +15 and -15V have to be there always together. Be careful not to shorten one rail.
7. When measuring voltages on soldered chips, esp. the AMP - be careful not to shorten a -15V or +15V with a neighbor pin. It will kill the AMP.
8. Connect the 0R (or set jumpers) and measure the output voltage on headphone connector. It should not have a high voltage (not in V, just few mV). Otherwise an OP could be dead or a shortcut on analog traces.
9. Testing the board in operation needs an I2S source: if you have an *USB to I2S* solution (e.g. XMOS), an FPGA (with design to generate I2S signal) or Raspberry Pi with extended Rasbian kernel (I2S driver) then you should be able to listen to sound on headphone connector.
  - The suggested 0R (or jumpers) are for 24bit I2S. The sample rate is recognized automatically by the DAC (48/96/192 Khz). The SCK signal is jumper-ed to be derived from BCK (for RPi).





## Stack with RPi

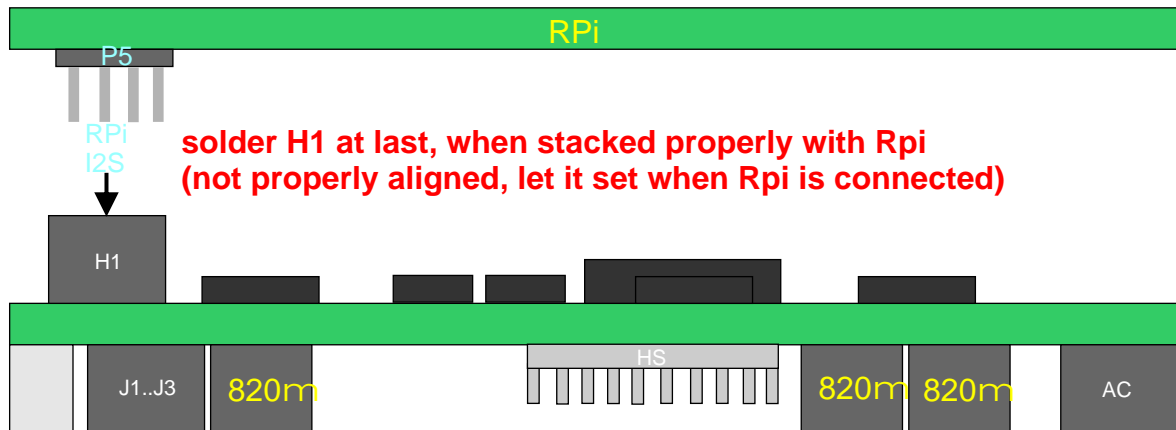

**solder H1 at last, when stacked properly with Rpi  
(not properly aligned, let it set when Rpi is connected)**

**mount AC connectors on bottom side  
of PCB, when stacked with RPi**

# How to solder the LDOs (QFP)?

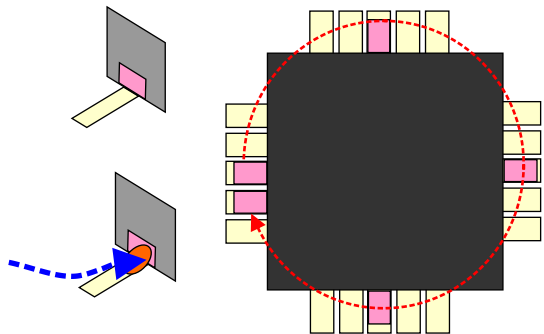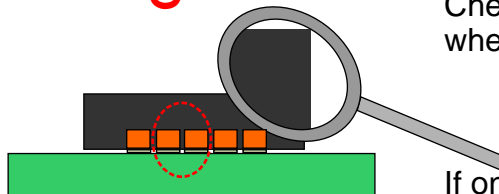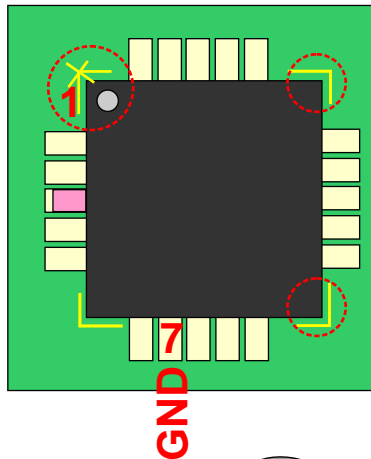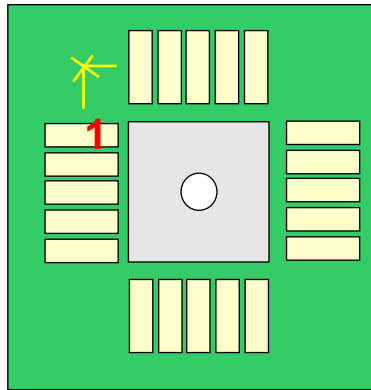

**Soldering the LDOs is the most complicated task** (QFP package, all connections under the package, also power pad). It is assumed that soldering without a head gun will be done.

Based on my experiences:

- use a magnifying glass, at best a **microscope**

- use SMD **No-Clean Paste Flux** (e.g. CHIPQUIK SMD291/10cc)

- keep the PCB clean, remove flux and dirt properly: I have seen LDO failing due to remaining flux. Use Isopropanol to “wash” the board

Put some solder on all pads, except the center power pad (quite same amount on all).

Check the pin 1 orientation (see drawing). Att: after “washing” hard to see the markers on package.

Provide the flux.


Place the LDO in approx. position.

Use magnifying glass or microscope to align the LDO. **All four sides are important** and the IC pads have to be above the PCB traces in a quite perfect position.

Solder just one pin. Provide solder so that it can flow a bit under the package or touch the small copper spot at the package side.

With just one pin soldered - check all pads on all sides under microscope. At best: turn the PCB a bit vertical in order to see the side of the package.

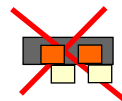Check if the small copper pad on the side is almost exactly adjusted above the PCB. Check, when you would provide solder - could it shorten neighbor pins?



**at all four sides**


If one of the side is not properly aligned, use solder tool on soldered pin and move the package smoothly into right direction. The yellow markers can guide you but they might not be accurate enough to solder just after aligning package based on these.

The gap between package and the yellow silk screen masks should be quite the same on all corners.


If the LDO is properly aligned on all sides - solder all remaining pins. You should rotate, change to next side pin for pin in order to avoid thermal stress on the package.

Suggestion: use flux so that the solder can flow under the package. Always use the solder tool with movement towards the package, try to touch the small copper pad at the side and to connect the solder with it.

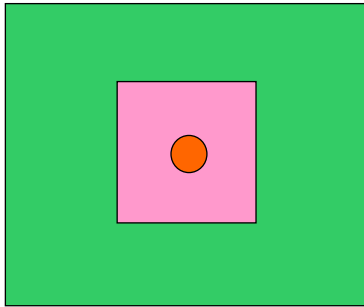Check for shortcuts and flux/dirt between the pins.



**Bottom**

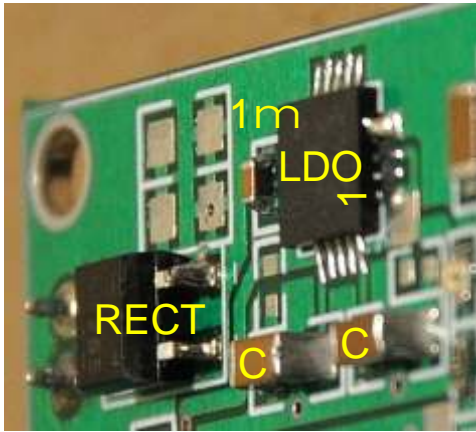

## Power Pad

After all LDOs were soldered, checked and they work properly, you can (optional) solder the power pad. The power pad properly connected with the PCB is “just” for thermal reasons (e.g. if a high input voltage is provided on AC and a large heat dissipation due to large In-Out voltage difference, e.g. >1V).

You can provide solder from the backside of the PCB. Use a solder tool with a bit higher power (e.g. 25W or 40W if you keep time short).

Provide enough solder so that it can flow in and through the hole. The flux will evaporate and the solder in the hole might not be perfect. Try several times until a nice result, the hole quite filled with solder. But avoid to overheat the PCB and IC, make breaks between trials.

**Do not use too much solder**, just to fill the hole. It could create shortcuts under the package which cannot be seen. There is no need to fill entire hole to the top (too much). Is the hole properly closed, even it looks like a valley, it should be fine.

Check the LDO again.

## Check the LDOs

Best practice:

Measure the resistance on the pad traces against ground. It should be in the range of KOhms, except on those which are intended to be grounded.

Measure the resistance between neighbored pads: there should not be a shortcut (except: two pins are connected together for input, output or ground). Take it as a shortcut if you see a resistance in Ohm range, e.g. even ~100 Ohm.

Measure the resistance of the input traces (pad 15 + 16, 20 + 1) against ground. Especially the input resistance should be in Kohms.


When you power the LDOs, limit the current (~50 mA) and increase voltage smoothly from 0V until max. 20V. Check if the LDO limits the voltage at intended output voltage (+15V, -15V, +5V, +3.3V, with some acceptable tolerance, e.g. 14.7 .. 15.3V).

If the regulated output voltage is too slow then one of the voltage setting pads is grounded (shortcut). If it is too high or there is not a regulation with max. 20V input then voltage setting pins intended to be grounded are not connected properly. Try to resolder pads again.

Observe the output voltage if it is stable, esp. it is not following the input voltage (e.g. 20V resulting in 19V output, should stop at ~15V). The output voltage should not oscillate (jump). Often the 1mF Cap is not connected properly or some flux/dirt left between pads.

If something fails: try to resolder pads, check all again, remove flux and dirt. Check if all capacitors are connected properly, esp. the 1mF and the 22mF or 47mF Caps at input and output. Watch out for weak solder spots or potential shortcuts. Check also the LDO package from the side with a microscope if there could be a short directly at the package corner, under the package.


# Block Diagram (PCB blocks)

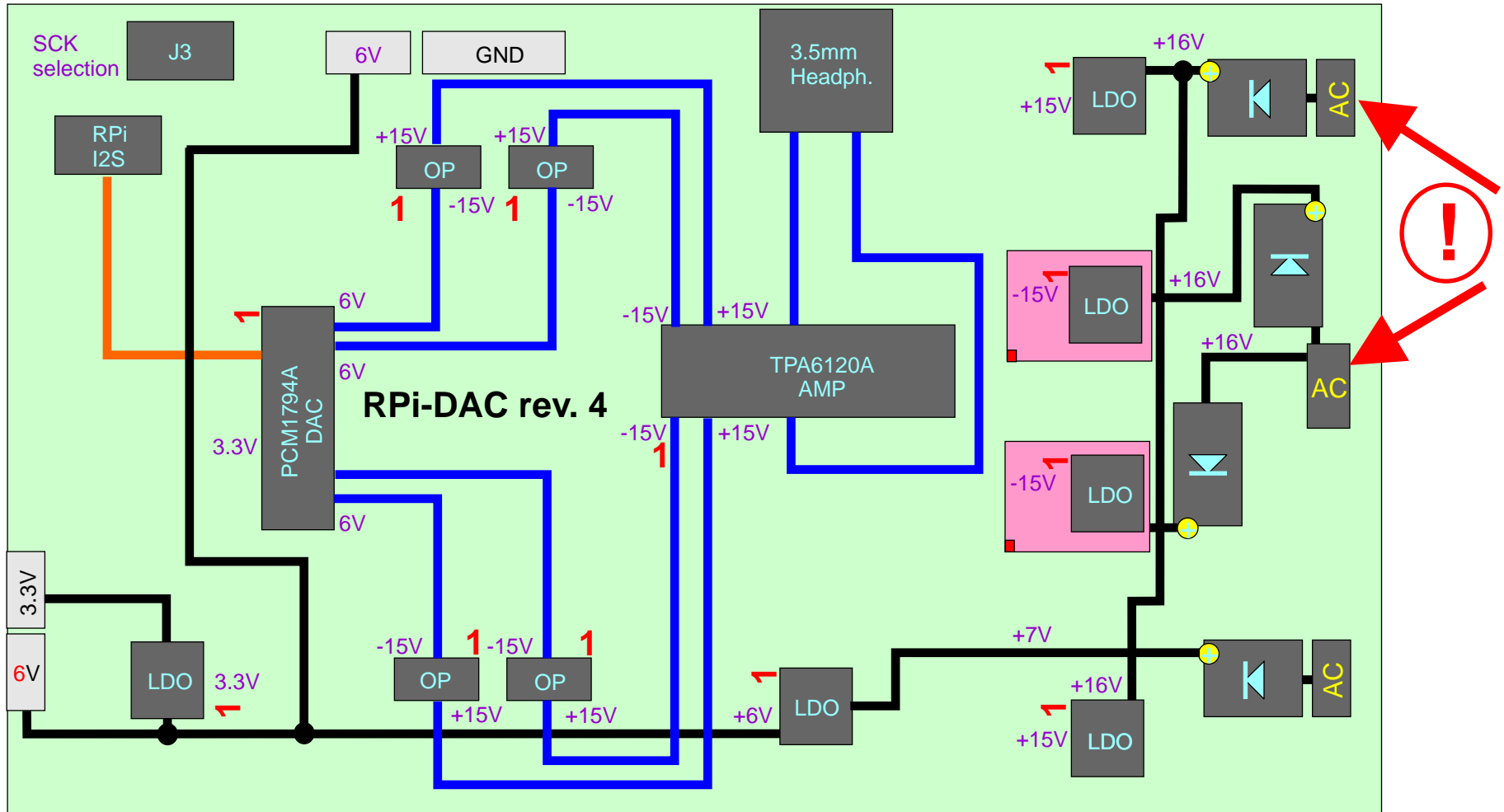

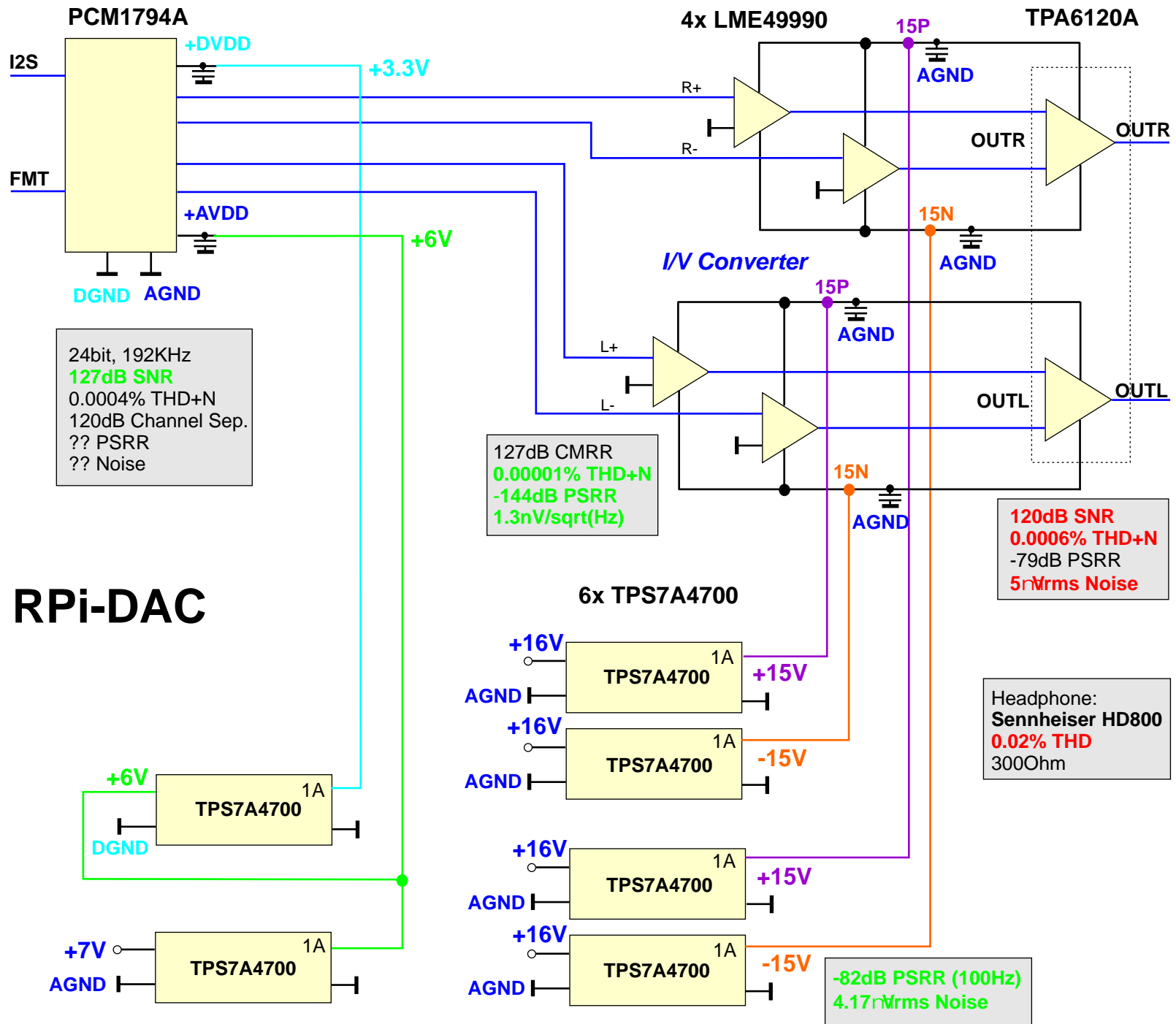
**After OPs and TPA6120 are soldered - always apply + and - 15V, never just one rail. Use AC with separate coils (no center tap or DC without common GND).**

For the schematics: please check out <http://www.tjaekel.com/T-DAC/schematics.html>





# RPi-DAC

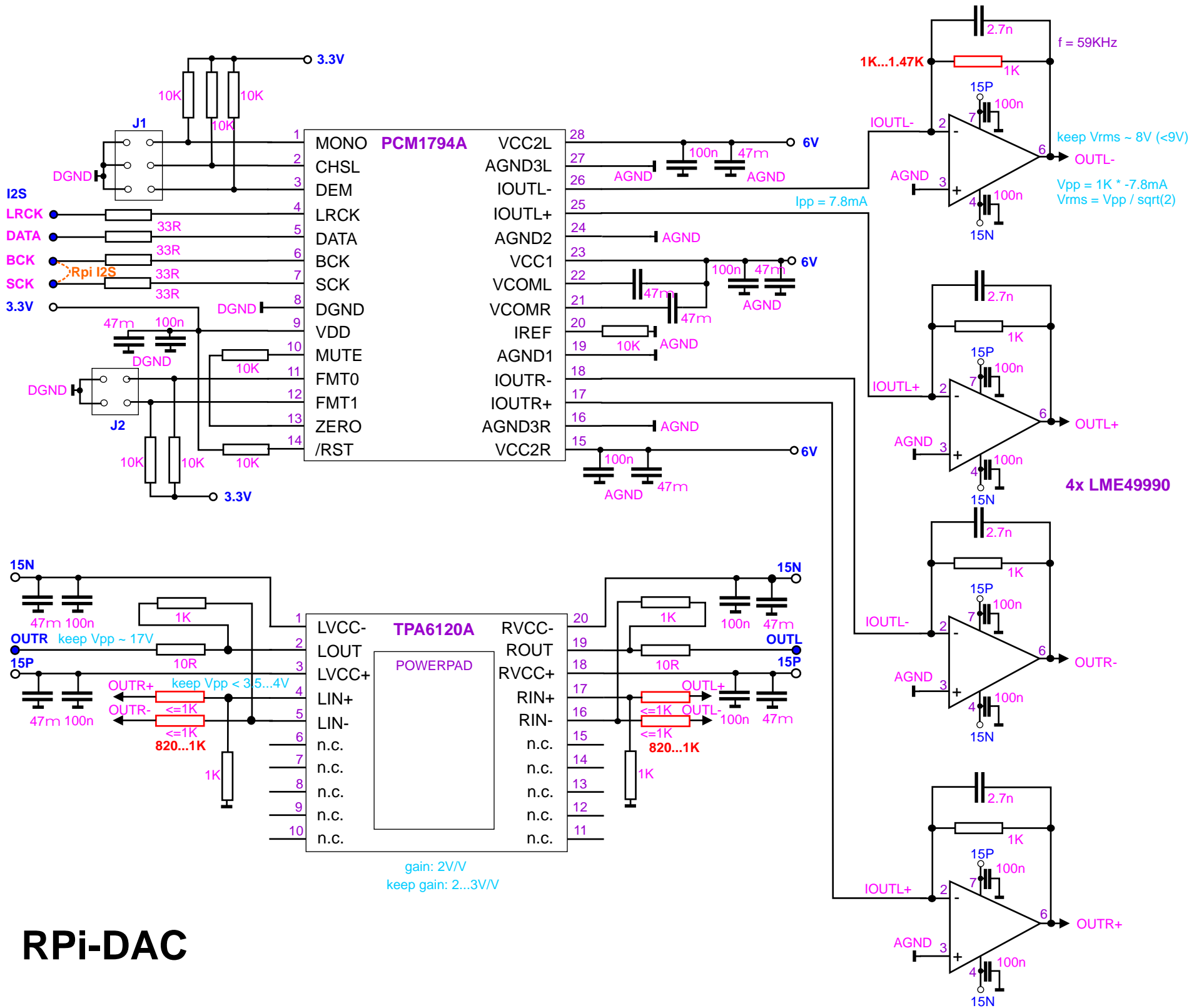

# RPi-DAC

# Pictures

